 


# Computer Organization and Architecture Laboratory, Autumn 2021

Assignment 1 - Neha Dalmia (19CS30055) and Rajat Bachhawat(19CS10073)

## Problem 1

### 1a : Half Adder




**Circuit Diagram of Half Adder**

**Truth Table for Half Adder**

a	b	sum = a ^ b	carry = a & b
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

### 1b : Full Adder

 


**Circuit Diagram for Full Adder implemented using Half Adders**


**Truth Table for Full Adder**

a	b	carry_in	$\text{sum} = a \oplus b \oplus C_{in}$	$\text{carry} = (a \& b) \mid (C_{in} \& (a \oplus b))$
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1


1c : n-bit Ripple Carry Adder Speeds

 

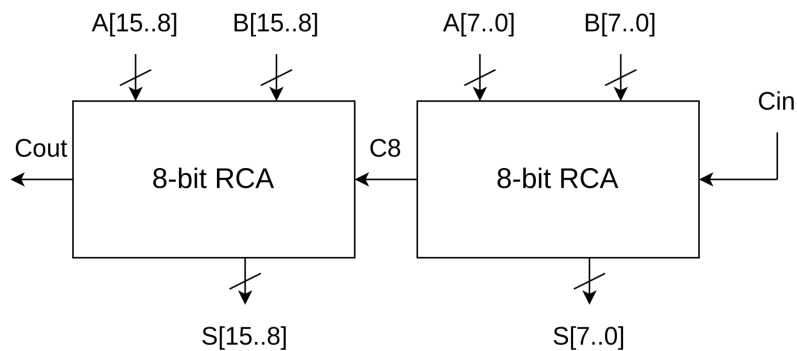
**Circuit Diagram for 8-bit Ripple Carry Adder implemented using full adders**



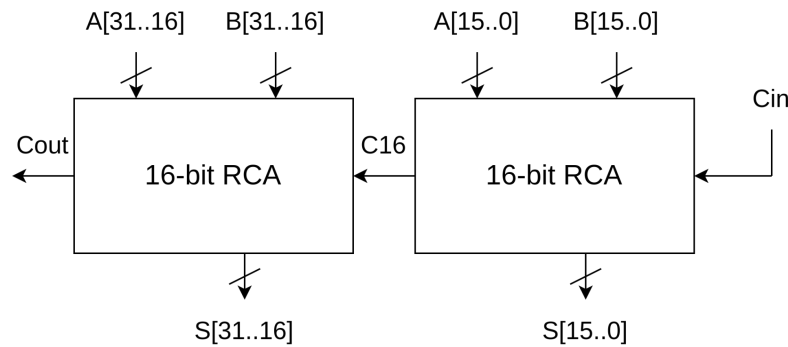**Circuit Diagram for 16-bit Ripple Carry Adder implemented using 8-bit RCAs**



 **Circuit Diagram for 32-bit Ripple Carry Adder implemented using 16-bit RCAs**



**Circuit Diagram for 64-bit Ripple Carry Adder implemented using 32-bit RCAs**

### Comparison of the various n-bit RCAs

	8-bit RCA	16-bit RCA	32-bit RCA	64-bit RCA
<b>Longest Delay</b>	9.949ns	18.717ns	36.253ns	71.325ns
<b>Number of Slice LUTs</b>	40	80	160	320
<b>Number of Bonded IO Buffers</b>	26	50	98	194
<b>Levels of Logic</b>	36	70	138	274

As the number of bits increases, the delay also increases mainly because of the **critical path - the rippling of the carry**.

### 1d : Subtraction using RCA

In order to perform  $a - b$ , we can write it as

$$\begin{aligned}
 & a + (-b) \\
 &= a + (2\text{s complement of } b) \\
 &= a + (1\text{s complement of } b) + 1
 \end{aligned}$$


where the 1s complement of  $b$  is obtained by inverting every bit of  $b$ .

Thus, we pass every bit of  $b$  through a NOT gate to get the inverse of  $b$ . In order to do the addition of 1, we can set the **initial carry to 1** in our RCA. This way, we get  $a + (\text{inverse of } b) + 1$  using an RCA.

In order to perform a subtraction of two  $n$  bit numbers, we can ripple in a series of  $n$  full adders to make an  $n$  bit RCA, and use it to perform the addition of  $a + (1\text{s complement of } b) + 1$  by setting the input carry to 1 instead of 0 and complementing bits of  $b$  using NOT gates. Thus, subtraction can be performed using addition using the 2s complement method. We do not have to perform two additions to add the extra 1 as it can be passed as the carry.

## Problem 2

### 2a : 4-bit Carry Lookahead Adder

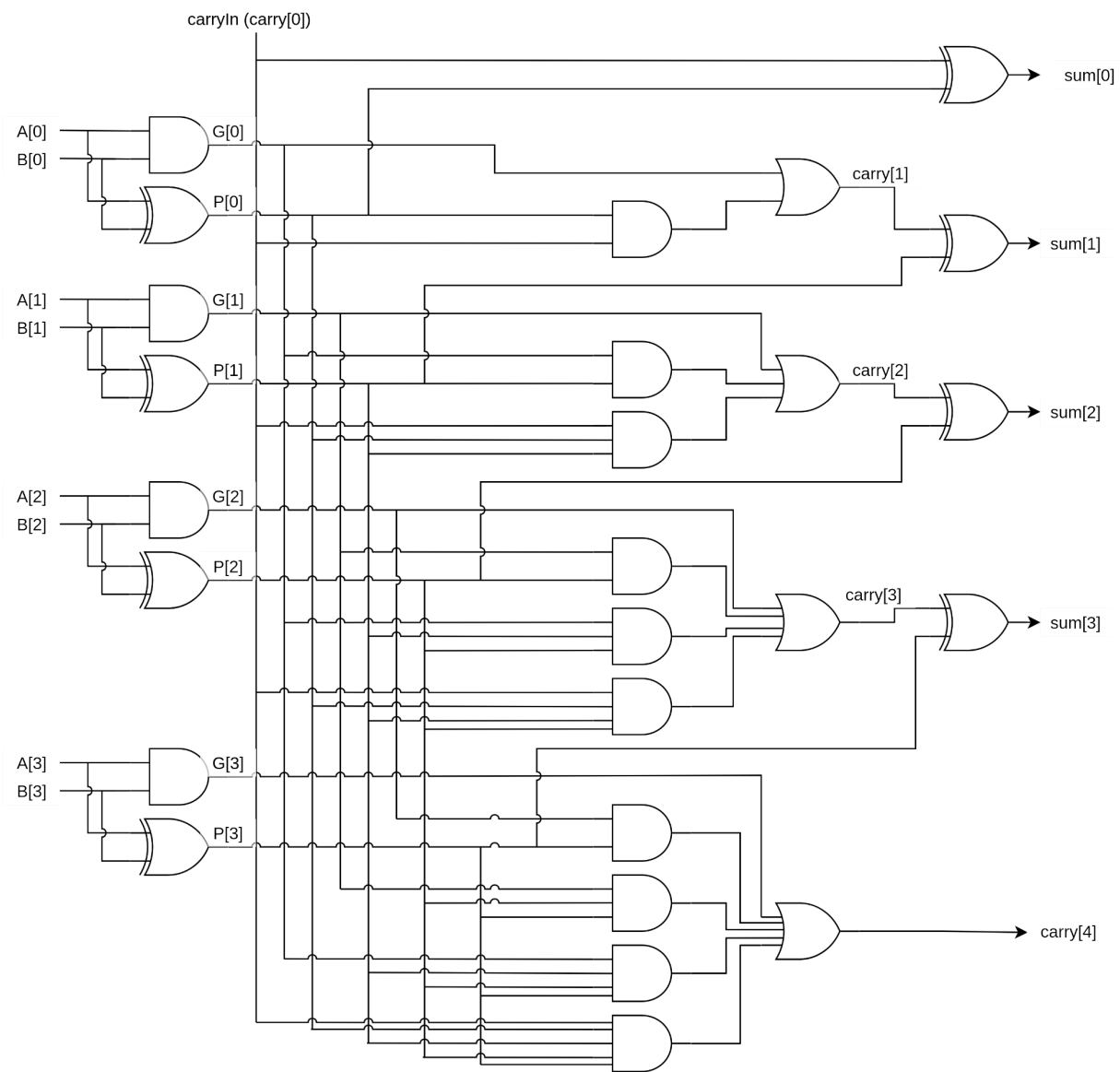

**Design of the 4-bit CLA**

#### Inputs:

$A[3..0]$ ,  $B[3..0]$ ,  $C_0$  (input carry)

## Outputs:

Sum[3..0] : Sum of A[3..0] and B[3..0]  
C4 (Output carry)

P[0..3] = Propagate signals  
G[0..3] = Generate signals  
carry[1..4] = Generated carry bits

**Equations** for the generate and propagate signals along with sum:

$P[i] = A[i] \wedge B[i]$ , for  $0 \leq i \leq 3$   
 $G[i] = A[i] \& B[i]$ , for  $0 \leq i \leq 3$   
 $sum[i] = P[i] \wedge carry[i]$ , for  $0 \leq i \leq 3$

Boolean equations of the Look-ahead carry generation for the 4 carry bits, **C1, C2, C3, and C4** :

carry[0] = input carry  
 $carry[i+1] = G[i] \mid (P[i] \& carry[i])$ , for  $0 \leq i \leq 3$

More specifically, on expanding:


$carry[1] = G[0] \mid (P[0] \& carry[0])$   
 $carry[2] = G[1] \mid (P[1] \& G[0]) \mid (P[1] \& P[0] \& carry[0])$   
 $carry[3] = G[2] \mid (P[2] \& G[1]) \mid (P[2] \& P[1] \& G[0]) \mid (P[2] \& P[1] \& P[0] \& carry[0])$   
 $carry[4] = G[3] \mid (P[3] \& G[2]) \mid (P[3] \& P[2] \& G[1]) \mid (P[3] \& P[2] \& P[1] \& G[0]) \mid (P[3] \& P[2] \& P[1] \& P[0] \& carry[0])$

2b : Comparison of 4-bit CLA with 4-bit RCA

	4-bit RCA	4-bit CLA
Longest Delay	5.565ns	2.123ns
Number of Slice LUTs	20	9
Levels of Logic	20	4

**Hence, the 4-bit CLA is much faster than the 4-bit RCA.** The reason for this is that we have eliminated the rippling of carry from one bit to another by introducing generate and propagate signals (and computing them in an optimised way using multiple levels of **lookahead circuit**) which speed up the process of carry generation and propagation through the circuit.

## 2c (i) : Augmented 4-bit CLA

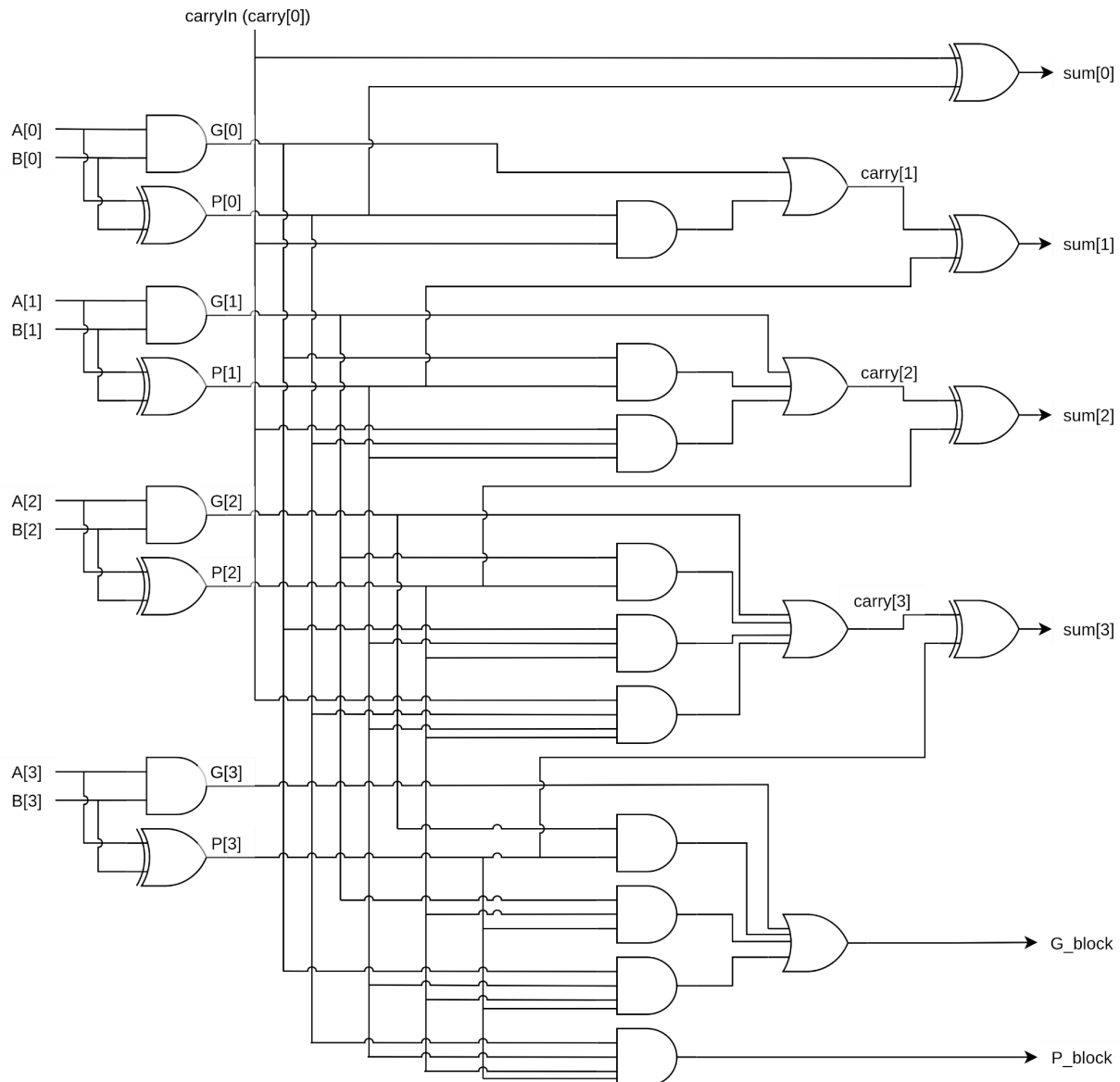

### Design of the augmented 4-bit CLA

In this case, instead of returning the carry out we give the **block propagate and generate** as output which are then used by the carry lookahead unit. This modular design can be used to make 16, 32 and 64 bit adders by combining the block propagate and generate from the lower levels instead of waiting for the carry to ripple out every time.

#### Inputs:

A[3..0], B[3..0], C0 (input carry)

#### Outputs:

Sum[3..0] : Sum of A[3..0] and B[3..0]

P\_Block : Block Propagate

G\_Block : Block Generate

P[0..3] = Propagate signals

$G[0..3]$  = Generate signals  
 $carry[1..4]$  = Generated carry bits

**Equations** for the generate and propagate signals:

$$P[i] = A[i] \oplus B[i], \text{ for } 0 \leq i \leq 3$$

$$G[i] = A[i] \& B[i], \text{ for } 0 \leq i \leq 3$$

**Boolean equations** of the Look-ahead carry generation for the 4 carry bits, C1, C2, C3, and C4:

$carry[0]$  = input carry

$$carry[i+1] = G[i] \mid (P[i] \& carry[i]), \text{ for } 0 \leq i \leq 3$$

More specifically, on expanding:

$$carry[1] = G[0] \mid (P[0] \& carry[0])$$

$$carry[2] = G[1] \mid (P[1] \& G[0]) \mid (P[1] \& P[0] \& carry[0])$$

$$carry[3] = G[2] \mid (P[2] \& G[1]) \mid (P[2] \& P[1] \& G[0]) \mid (P[2] \& P[1] \& P[0] \& carry[0])$$

No need to calculate  $c[4]$  as the LCU does that using P\_Block and G\_Block.


$$sum[i] = P[i] \oplus carry[i], \text{ for } 0 \leq i \leq 3$$

Calculation of Block Propagate and Generate for the entire 4-bit block (independent of  $carry[0]$ ):

$$P\_block = P[3] \& P[2] \& P[1] \& P[0]$$

$$G\_block = G[3] \mid (P[3] \& G[2]) \mid (P[3] \& P[2] \& G[1]) \mid (P[3] \& P[2] \& P[1] \& G[0])$$


2c (ii) : 16-bit CLA with Lookahead Carry Unit

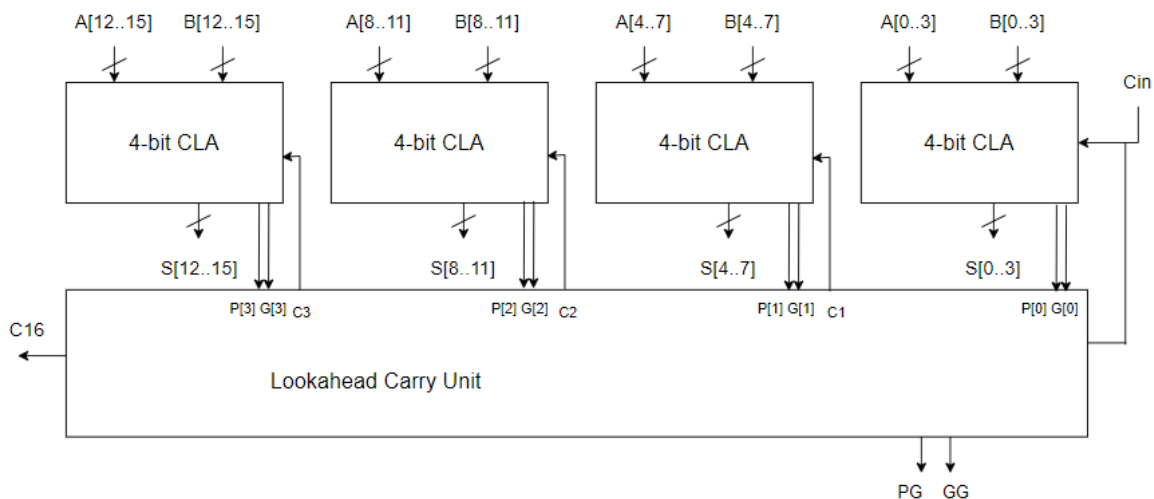

**Design 1 : Design of 16-bit CLA using block propagates and block generates passing through a second layer of lookahead**

Instead of waiting for the carry to ripple out from the 4-bit blocks, the LCU simultaneously calculates these carries using the P\_Block and G\_block from the 4-bit CLAs. Then it creates its own P and G blocks which can be used by higher order adders.
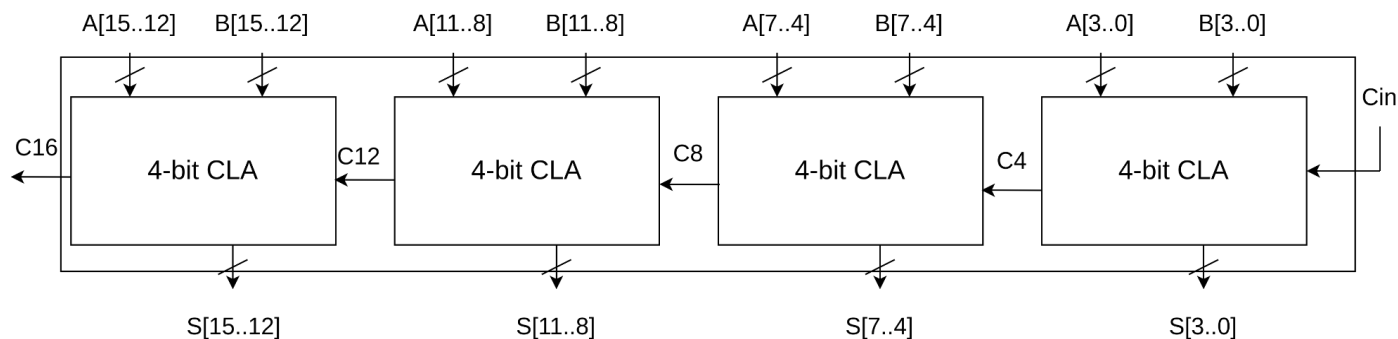
### 2c (iii) : Comparison of Delays between the two versions of 16-bit CLA



### Design 2 : Design of 16-bit CLA by rippling carries from the 4-bit CLA blocks

	16-bit CLA without Lookahead Carry Unit	16-bit CLA with Lookahead Carry Unit
Longest Delay	6.167ns	5.243ns
Number of Slice LUTs	16	29
Number of Bonded IO Buffers	50	52
Levels of Logic	14	11

Hence, the inclusion of the Lookahead Carry Unit improves the speed of the 16-bit CLA in comparison to cascaded 4-bit CLA structure where the carry bits are rippled in. The reason is that the former has an extra level of lookahead circuit which optimises the generation/propagation of carry bits even more.

### 2c (iv) : Comparison between the 16-bit CLA and the 16-bit RCA

	16-bit Ripple Carry Adder	16-bit Carry Lookahead Adder
Longest Delay	18.717ns (Levels of Logic = 70)	5.243ns (Levels of Logic = 11)
Number of Slice LUTs	48 / 63400	29 / 63400



<b>Number of Bonded IO Buffers</b>	50 / 210	52 / 210
<b>Number of LUT-FF Pairs used</b>	48	29
<b>Number of Occupied Slices</b>	48 / 15850	14 / 15850

Hence, we see that:

1. The **lookup table (LUT) cost** of the 16-bit CLA is much **lesser** in comparison to the 16-bit RCA.
2. The **speed** of the 16-bit CLA is much **greater** (as delay is lesser) in comparison to the 16-bit RCA.

The reason for this is that we have eliminated the rippling of carry from one bit to another by introducing generate and propagate signals (and computing them in an optimised way using multiple levels of **lookahead circuit**) which speed up the process of carry generation and propagation through the circuit.